

Industrial Controls Training System

## **Courseware Sample**

39163-F0

***Lab-Volt***<sup>®</sup>





INDUSTRIAL CONTROLS TRAINING SYSTEM

COURSEWARE SAMPLE

by  
the Staff  
of  
Lab-Volt Ltd.

**Copyright © 2007 Lab-Volt Ltd.**

All rights reserved. No part of this publication may be reproduced, in any form or by any means, without the prior written permission of Lab-Volt Ltd.

**Printed in Canada  
January 2009**

# Table of Contents

<b>Introduction</b> .....	V
<b>Courseware Outline</b>	
Basic Controls .....	VII
<b>Sample Exercise Extracted from Basic Controls</b>	
Exercise 3-4 Reversing Starters .....	3
<b>Instructor Guide Sample Extracted from Basic Controls</b>	
Exercise 2-2 Symbols, Designations, and Diagrams .....	15



# Introduction

The Lab-Volt Industrial Controls Training System, Series 8036, has unique controls training capabilities, which are enhanced by its modularity and its instructor-inserted faults. The system allows the student to select and mount control devices to form typical control circuits, and to troubleshoot them once a fault is inserted.

The Industrial Controls Training System is divided into four levels, each level being further divided into specific topics that deal with various aspects of industrial controls equipment operation. The Basic Controls system, Model 8036-1, provides the student with a complete basic training in motor controls. The Programmable Logic Controller system, Model 8036-2, introduces the use of PLCs to control the motor operation. The Motor Drives system, Model 8036-3, introduces the use of the DC and AC drives. The Sensors system, Model 8036-4, introduces photoelectric and proximity switches.



# Courseware Outline

## **BASIC CONTROLS**

### **Unit 1 Basic Principles of Motor Control**

- Ex. 1-1 Lockout/Tagout Procedure
- Ex. 1-2 Control Panel Devices
- Ex. 1-3 Manual Starters
- Ex. 1-4 Contactors and Control Relays
- Ex. 1-5 Current Protection Devices

### **Unit 2 Circuit Layout and Specifications**

- Ex. 2-1 Specifications Reading
- Ex. 2-2 Symbols, Designations, and Diagrams

### **Unit 3 Basic Control Circuits**

- Ex. 3-1 Motor Starters
- Ex. 3-2 Two-Wire and Three-Wire Controls
- Ex. 3-3 Manual Reversing Starters
- Ex. 3-4 Reversing Starters
- Ex. 3-5 Multiple Push Buttons

### **Unit 4 Jogging Control Circuits**

- Ex. 4-1 Friction Brakes
- Ex. 4-2 Motor Starters with Jogging
- Ex. 4-3 Reversing Starters with Jogging

### **Unit 5 Reduced AC Voltage Starters**

- Ex. 5-1 Primary Resistor Starters
- Ex. 5-2 Soft Starters

### **Unit 6 Time Relay Circuits**

- Ex. 6-1 Time Relays
- Ex. 6-2 Plugging with Time Relays
- Ex. 6-3 Primary Resistor Starters with Time Relays

- |                   |          |  |
|-------------------|----------|--|
| <b>Appendices</b> | <b>A</b> | <b>Equipment Utilization Chart</b>                               |
|                   | <b>B</b> | <b>Diagram Symbols</b>   |
|                   | <b>C</b> | <b>Motor Frames Charts</b>                                       |
|                   | <b>D</b> | <b>Basic Setup and Lockout/Tagout Procedures</b>                 |
|                   | <b>E</b> | <b>Brake Motor, Inertia Wheel, and Safety Guard Installation</b> |
|                   | <b>F</b> | <b>Brake Motor Characteristics</b>                               |
|                   | <b>G</b> | <b>Glossary</b>  |



Sample Exercise  
Extracted from  
Basic Controls





# REVERSING STARTERS

### EXERCISE OBJECTIVE

- Implement magnetic reversing starters.
- Understand the principles of mechanical and electrical interlocking.

### DISCUSSION

As you have seen in the previous exercise, reversing rotation direction of a three-phase motor is usually done by interchanging any two power lines. When the equipment is sufficiently rugged, motor line reversal can be accomplished while the motor is running at full speed. This has a major advantage: a counter torque is developed and the motor stops faster. This motor braking method is called **plugging**.

When phase reversal is executed in magnetic circuits, one contactor is used for each direction. But a short-circuit can occur if the two contactors are energized at the same time. Look at the Figure 3-9 power circuit, for example. If all contacts of the F and R contactors close, lines 1 and 2 will be short-circuited. That is the reason why forward and reverse contactors are usually electrically and/or mechanically interlocked together.

#### Push button interlocking

Avoiding simultaneous actuation of two contactors can be done electrically, by way of push button interlocking.

When the FWD push button in Figure 3-9 is pressed, the coil (F) is energized and the related holding contact closes. If the REV push button is pressed while the motor is running in the forward direction, the forward control circuit de-energizes. At the same time, the reverse contactor (R) is energized and held closed, making the motor run in the reverse direction. Note that it is not necessary to press the STOP push button to reverse direction. This fact facilitates plugging.

If the FWD and REV push buttons are simultaneously activated, both contactors will stay open. That is because push button NC contacts open the control circuit completely, thereby forcing contactor coils to de-energize.

However, if a contactor coil is stuck closed or does not open fast enough, there can still be a short-circuit when the other coil is activated.

## REVERSING STARTERS

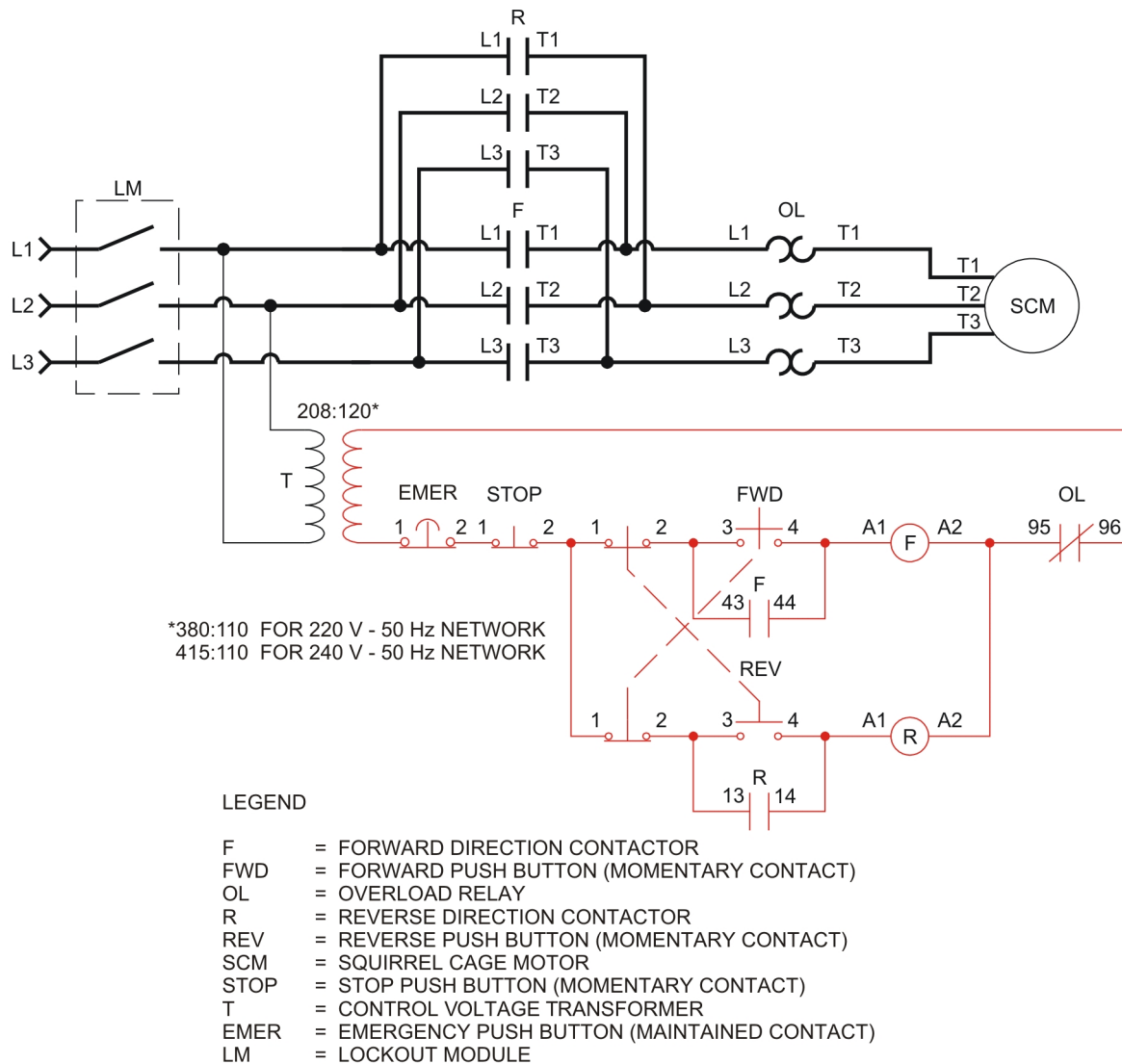


Figure 3-9. Push button interlocking circuit.

### Mechanical Interlocking

A mechanical lever is another manner of preventing both starter coils from being energized simultaneously. Figure 3-10 displays the mechanical interlock located between the two contactors of the Dual Contactors, Model 3119.

## REVERSING STARTERS

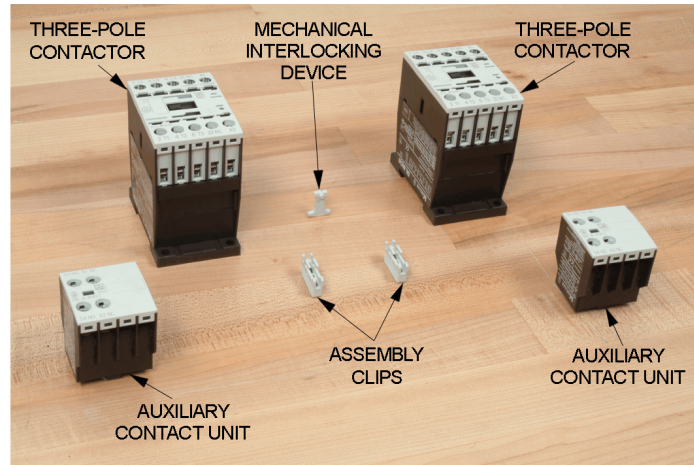


Figure 3-10. Mechanical interlocking.

If you refer to the Figure 3-11 circuit, a mechanical interlock (in dashed lines) is located between the two contactor coils. When one of the two contactors is energized, the contacts of the other contactor are mechanically maintained, even if the second coil is energized. This method provides a level of security against short-circuits resulting from stuck contactors. This explains why mechanical interlocks are so common in the industry.

## REVERSING STARTERS

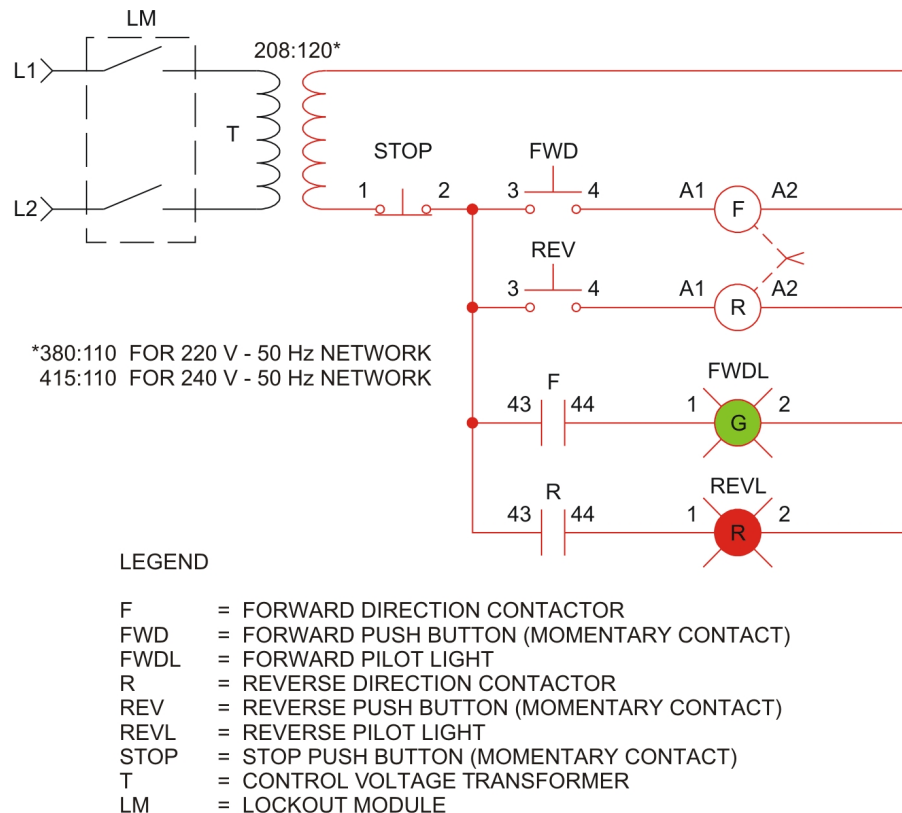


Figure 3-11. Dual contactors testing circuit.

### Procedure Summary

In the first part of this exercise, you will set up a reversible starter circuit with push button interlocking and verify that this circuit enables changing of motor direction. You will also observe that motor direction reversing can be accomplished without having to press the STOP push button, to stop the motor faster. You will then verify that both contactors remain de-energized if the operator accidentally presses the two push buttons. Finally, you will simulate a stuck contactor to see that push button interlocking does not protect against short-circuits resulting from that type of trouble.

In the second part of this exercise, you will study, with the assistance of pilot lights, how a mechanical interlock operates. By manually applying pressure on the dual contactors plungers, you will check that it is not possible to activate both contactors at the same time. You will then visualize that, when both coils are powered, only the first contactor has its related contacts closed.

In the last part of this exercise, you will connect a reversing starter with push button and mechanical interlocks. You will see that this circuit, like the push button interlock circuit, enables motor direction reversal and opens completely when both push buttons are pressed. You will also discover that the mechanical interlock included adds protection against stuck contactors.

# REVERSING STARTERS

## EQUIPMENT REQUIRED

Refer to the Equipment Utilization Chart in Appendix A to obtain the list of equipment required for this exercise.

## PROCEDURE

### WARNING!



The AC Power Supply provides high voltages. Do not change any AC connection with the power on.

### Basic setup

- 1. Perform the Basic Setup and Lockout/Tagout procedures.

### Push button interlocking

- 2. Install the Brake Motor, Inertia Wheel, and Safety Guard.

Connect the circuit shown in Figure 3-9.

**Note:** Use one of the two contactors from the Dual Contactors, Model 3119, as the forward direction contactor, and the Contactor, Model 3127, as the reverse direction contactor, to make sure that there is no mechanical link between contactors.

- 3. Manually disengage the friction brake.

Perform the Energizing procedure.

Determine the motor rotation direction as you press the FWD push button.

- Clockwise     Counterclockwise

- 4. Press the STOP push button and observe the time taken by the motor to stop.

- 5. Determine the motor rotation direction as you press the REV push button.

- Clockwise     Counterclockwise

## REVERSING STARTERS

6. Compared to the forward operation, does the motor turn in the other direction?

Yes       No

**Note:** *The contactors are all AC-4 rated. This class allows for plugging operation (reversing direction of rotation from other than off condition).*

7. While the motor is running in the reverse direction, press the FWD push button until the motor halts. Press the STOP push button before the motor starts rotating in the opposite (forward) direction. Repeat if necessary.

**Note:** *Repeated motor starts and stops may cause the Overload Relay to trip.*

Did the motor stop slower or faster than with the STOP push button only?

Slower     Faster

8. When the FWD push button was pressed, why were both contactors (F and R) not activated at the same time, thereby causing a short-circuit?

---

---

---

9. What happens when you keep the FWD and REV push buttons pressed simultaneously?

---

---

10. Describe how the circuit operates while you simultaneously keep the FWD and REV push buttons pressed.

---

---

11. What happens if you do not release both push buttons simultaneously? Explain why.

---

---

## REVERSING STARTERS

12. Press the FWD push button to start the motor.

To simulate a stuck contactor, manually hold the forward contactor plunger down (using the tip of a pen), then press the REV push button. What happens?

---

---

13. Describe how the circuit operates while you simultaneously hold the forward contactor plunger down and press the REV push button.

---

---

14. Does push button interlocking offer a good protection against stuck contactors?

Yes     No

15. Perform the Lockout/Tagout procedure.

### Mechanical interlocking

16. Connect the circuit shown in Figure 3-11.

**Note:** Use the two contactors from the Dual Contactors module.

17. Perform the Energizing procedure.

18. Can you (manually) hold down completely the two contactor plungers simultaneously? Explain why.

---

---

19. When you press the FWD push button alone, which contactor coil is energized? (refer to the respective pilot lights)

F     R

## REVERSING STARTERS

- 20. When you press the REV push button alone, which contactor coil is energized? (refer to the respective pilot lights)
  - F    R
  
- 21. Does pressing the FWD and REV push buttons energize both contactor coils simultaneously?
  - Yes    No
  
- 22. When both push buttons are pressed, which contactor coil(s) energize(s), in regard to the order in which the corresponding push buttons were pressed?
  - The first    The second    Both    None
  
- 23. Perform the Lockout/Tagout procedure.

### Reversing starter with push button and mechanical interlock

- 24. Connect the circuit shown in Figure 3-9, this time using the two contactors from the Dual Contactors module.
  
- 25. Perform the Energizing procedure.
  - Determine the motor rotation direction as you press the FWD push button.
    - Clockwise    Counterclockwise
  
- 26. Press the STOP push button and wait for the motor to stop.
  
- 27. Determine the motor rotation direction as you press the REV push button.
  - Clockwise    Counterclockwise
  
- 28. While the motor is running in the reverse direction, press the FWD push button. Does the motor direction change? Explain what happens, considering that the circuit now contains a mechanical interlock.

---

---

---

## REVERSING STARTERS

29. Press both push buttons simultaneously, and determine which contactor(s) energize(s), in regards to the order in which the corresponding push buttons were pressed.

The first     The second     Both     None

30. Press the FWD push button to start the motor. To simulate a stuck contactor, manually hold the forward contactor plunger down (using the tip of a pen). Press the REV push button.

Does the motor still run in the forward direction? Explain why.

---

---

31. Does mechanical interlocking offer protection against stuck contactors?

Yes     No

32. Turn the individual power switch of the AC Power Supply off, disconnect the circuit, remove the magnetic labels, and return the equipment to the storage location.

### CONCLUSION

Reversing magnetic starters are built with two contactors, one per rotation direction. If both contactors are actuated at the same time, a short-circuit can occur. This is why electrical and/or mechanical interlocks are used.

Push button interlocking is an electrical means of disabling two contactors actuation. When a push button is pressed, the circuit controlling the other motor direction is automatically opened.

Mechanical interlocking uses a lever to artificially keep the second contactor de-energized, while the first coil is actuated. This method is more rugged in the way that it prevents short-circuits resulting from a stuck contactor.

Plugging is a method of making the motor brake faster. It is accomplished by reversing phases while the motor is running.

# REVERSING STARTERS

## REVIEW QUESTIONS

1. What is the purpose of interlocking in reversing starters?
  - a. Prevent any contactor from being energized
  - b. Prevent any contactor from being de-energized
  - c. Stop the motor in case of electrical overload
  - d. Prevent two contactor coils from being energized at the same time
  
2. How many contactors are necessary for reversing starters?
  - a. 2
  - b. 3
  - c. 4
  - d. 5 or more
  
3. What is the motor braking method called that uses the counter torque produced by reversing connections?
  - a. Inching
  - b. Plugging
  - c. Jogging
  - d. DC injection
  
4. In mechanical interlocking, which item prevents both coils from being actuated simultaneously?
  - a. Coil
  - b. Lever
  - c. Push button
  - d. Diode
  
5. In the Figure 3-9 circuit, which lines have been interchanged in the reverse mode compared to the forward mode?
  - a. Line 1 and line 2
  - b. Line 1 and line 3
  - c. Line 2 and line 3
  - d. Line 1 and line N

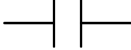





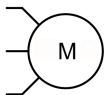
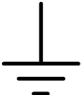
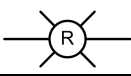
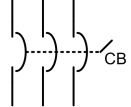
Instructor Guide Sample  
Extracted from  
Basic Controls



## EX. 2-2 SYMBOLS, DESIGNATIONS, AND DIAGRAMS

### ANSWERS TO PROCEDURE STEP QUESTIONS

□ 1.

ITEMS	SYMBOLS
Normally open contact	
Single throw toggle switch	
Diode	
Normally closed contact (IEC)	
Fixed resistor	
Relay operating coil	
Three-phase induction motor	
Earth ground	
Red indicating light	
3-pole manual circuit breaker	

# Basic Controls

- 2.
  - a. Time-delay opening contacts: TO or TDO
  - b. Overload: OL
  - c. Diode: D
  - d. Circuit-breaker: CB
  - e. Push button: PB
  - f. Ammeter: AM
  - g. Fuse: FU
  - h. Capacitor: C or CAP
  - i. Pressure switch: PS
  - j. Transistor: Q
  
- 3.
  - a. General transformer (control)
  - b. Normally closed, push button contact (stop button)
  - c. Normally open, push button contact (start button)
  - d. Normally open, push button contact (jog button)
  - e. Normally open contact (relay contact)
  - f. Normally open contact (contactor contact)
  - g. Normally open contact (relay contact)
  - h. Relay coil (main contactor coil)
  - i. Relay coil (relay coil)
  - j. Normally closed contact (overload relay contact)
  - k. Normally open contacts (main contactor power contacts)
  - l. Thermal overload elements
  - m. Squirrel-cage induction motor
  
- 4.

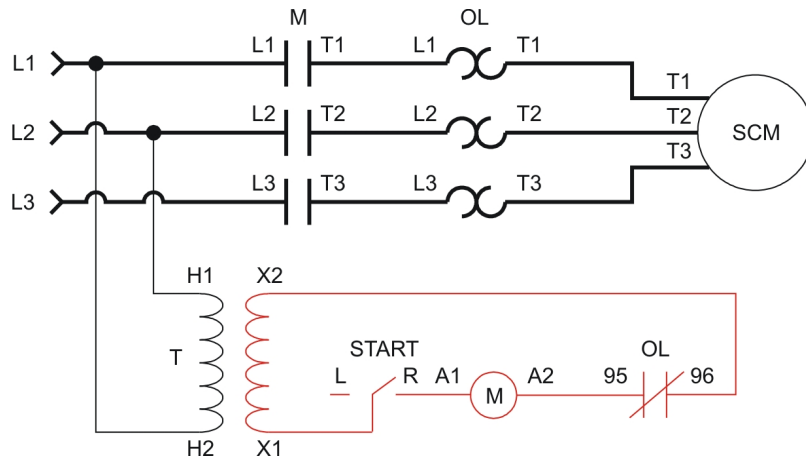


Figure 2-9. Schematic Diagram.

## ANSWERS TO THE REVIEW QUESTIONS

1.a; 2.b; 3.d; 4.b; 5.d.